
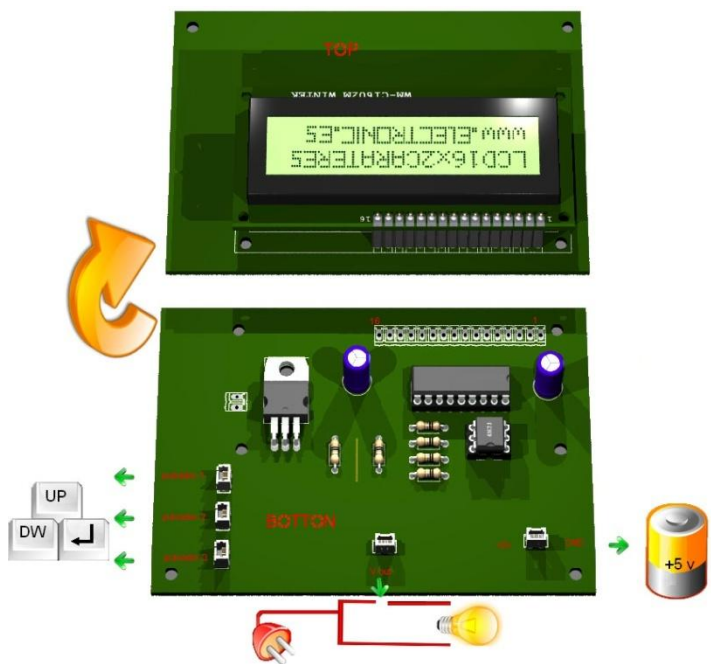


This circuit is thought for his functioning like control of time of gotten a sun stroke, his functioning is quite basic, one consists of 2 C.I.'s plates that he bears the microprocessor 16F628, and the other that the LCD, In program is basically we have 2 options in the menu ( Insoling, configuration ) the first is obvious, will maintain the light kindled according to the time stipulated by us ( the first time will be 00:00 ), seconds it configuration gets into mode and we will be able to adjust the time with the press buttons ( + , - ) according to be tenths minute, minute, tenths secondly or Second, the way out an optotriac makes itself intervening to 220vac. nutrition comes from 5Vcc.

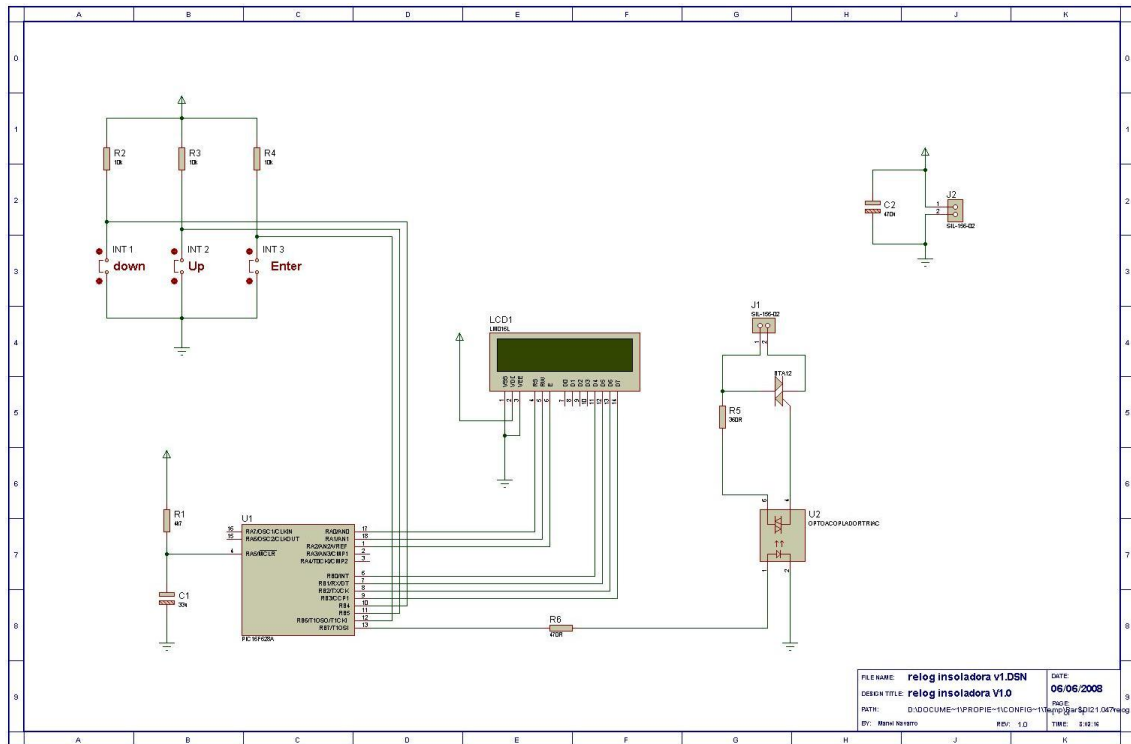

Scheme connection of the 2 printed circuit boards.

The schemes and program in HEX find them in [www.electronik.es](http://www.electronik.es)