

Gain of the Three Op Amp Instrumentation Amplifier

by Paul J. Miller

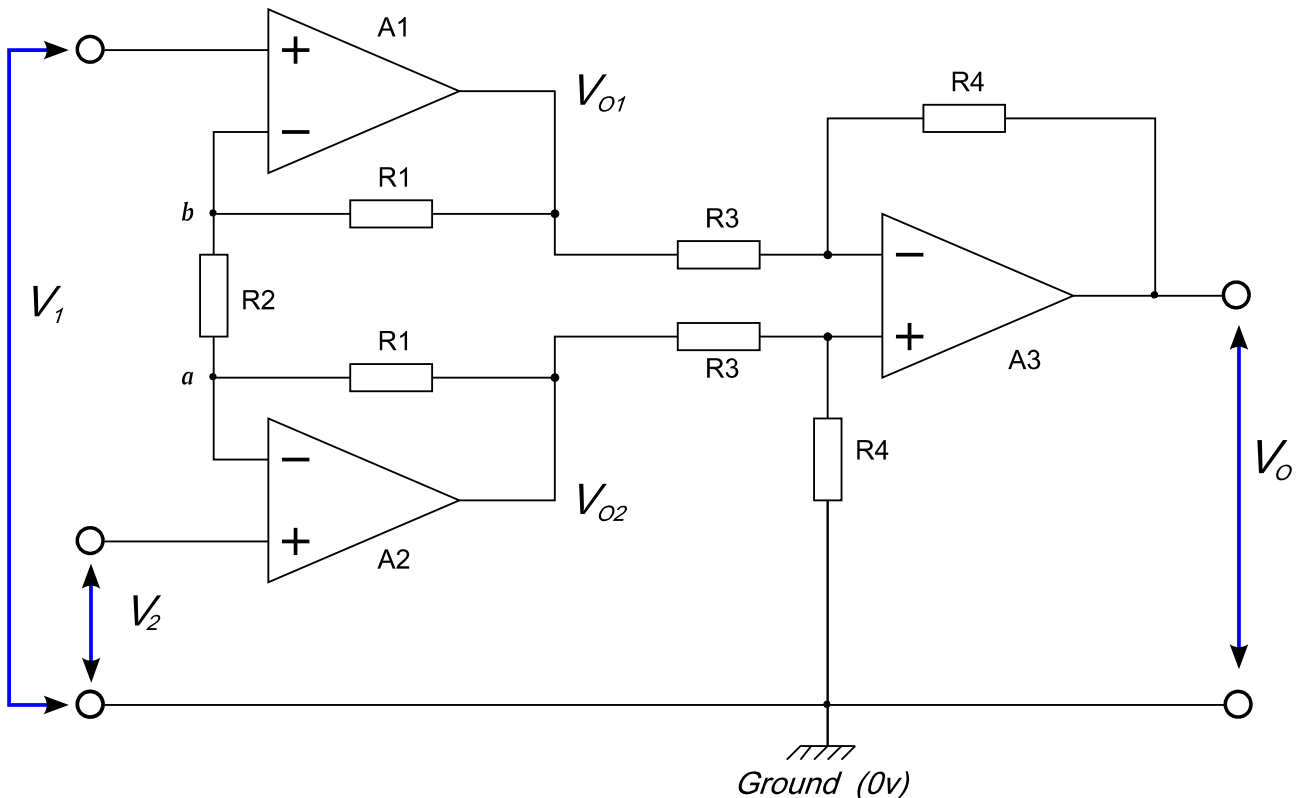


Figure 1.

Consider the amplifier illustrated in Figure 1.

The first stage is a balanced input, balanced output amplifier formed by A1 and A2 which amplifies the differential signal but passes the common mode signal without amplification. The second stage formed by A3 is a differential amplifier which largely removes the common mode signal.

The voltage V_{O1} consists of two components, the voltage due to V_1 and the voltage due to V_2 .

If $V_2 = 0$ then point *a* will be a virtual earth and amplifier A1 will act as a non inverting amplifier with a gain of

$$V_{O1} = V_1 \left(\frac{R1 + R2}{R2} \right)$$

If $V_1 = 0$ then point *b* will be a virtual earth and amplifier A1 will act as an inverting amplifier with a gain of

$$V_{O1} = - \left(\frac{R1}{R2} \right) V_2$$

the output from amplifier A1 with respect to ground (0v) will be

$$V_{o1} = \frac{R1+R2}{R2} V_1 - \frac{R1}{R2} V_2$$

$$V_{o1} = \frac{(R1+R2)V_1 - R1V_2}{R2}$$

$$V_{o1} = \left(\frac{R1}{R2} + 1\right) V_1 - \frac{R1}{R2} V_2$$

$$V_{o1} = \frac{R1}{R2} \{V_1 - V_2\} + V_1$$

Similarly the output from amplifier A2 with respect to ground will be

$$V_{o2} = \frac{R1}{R2} \{V_2 - V_1\} + V_2$$

These two voltages are fed into a differential amplifier A3, the gain of this amplifier is given by

$$V_o = \frac{R4}{R3} (V_{o2} - V_{o1})$$

If we substitute the equations for V_{o2} and V_{o1} we get

$$V_o = \frac{R4}{R3} \left(\left\{ \frac{R1}{R2} \{V_2 - V_1\} + V_2 \right\} - \left\{ \frac{R1}{R2} \{V_1 - V_2\} + V_1 \right\} \right)$$

We can simplify this

$$V_o = \frac{R4}{R3} \left\{ \frac{R1V_2}{R2} - \frac{R1V_1}{R2} + V_2 - \frac{R1V_1}{R2} - \frac{R1V_2}{R2} + V_1 \right\}$$

$$V_o = \frac{R4}{R3} \left\{ \frac{2R1V_2}{R2} + V_2 - \frac{2R1V_1}{R2} + V_1 \right\}$$

$$V_o = \frac{R4}{R3} \left(V_2 \left\{ 1 + \frac{2R1}{R2} \right\} - V_1 \left\{ 1 + \frac{2R1}{R2} \right\} \right)$$

$$V_o = (V_2 - V_1) \frac{R4}{R3} \left\{ 1 + \frac{2R1}{R2} \right\}$$

Therefore the differential gain G is

$$G = \frac{R4}{R3} \left\{ 1 + \frac{2R1}{R2} \right\}$$