

# BJT Bias

---


Copyright (c) 2012 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


Please send corrections (or suggestions) to [youngwlim@hotmail.com](mailto:youngwlim@hotmail.com).

This document was produced by using OpenOffice and Octave.

# Common Base (1)


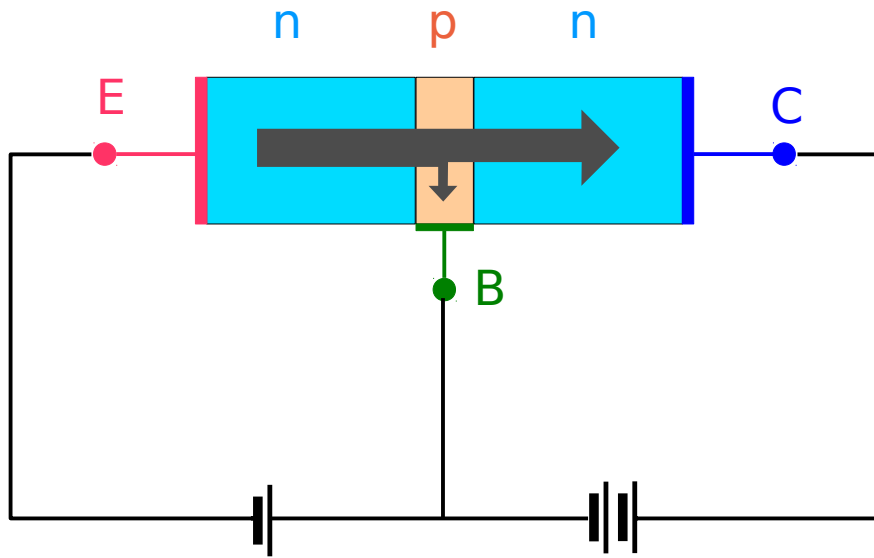


*Electron Flow*

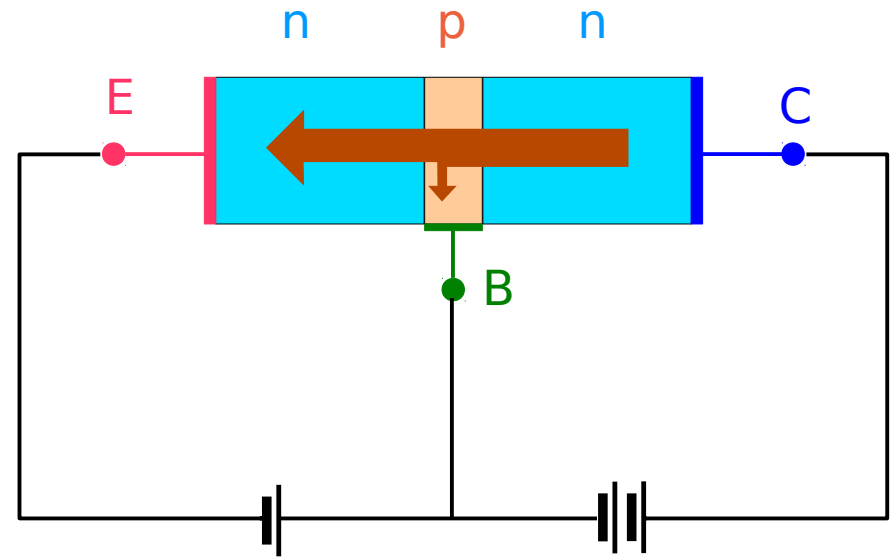


*Current Flow*


# Common Base (2)

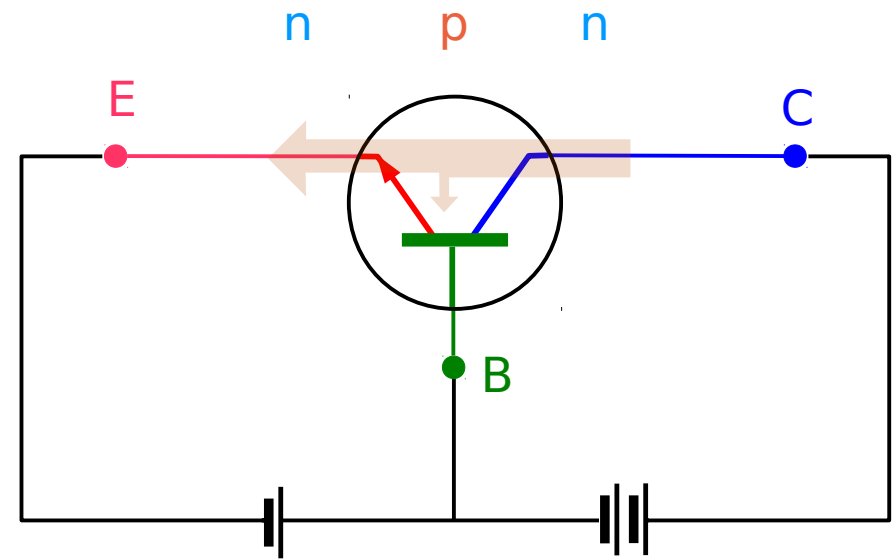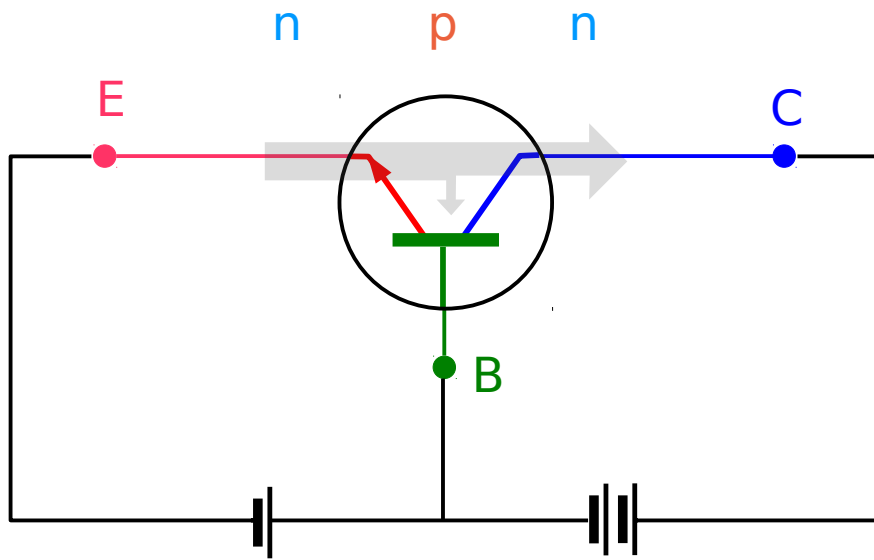


*Electron Flow*

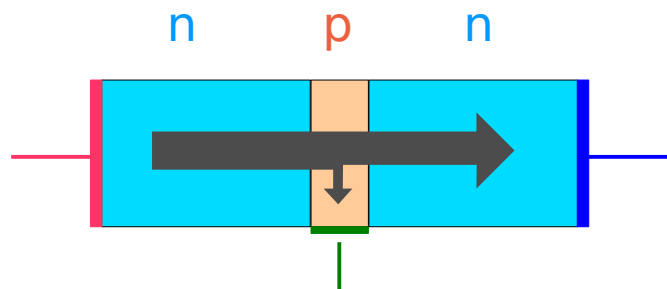


*Current Flow*

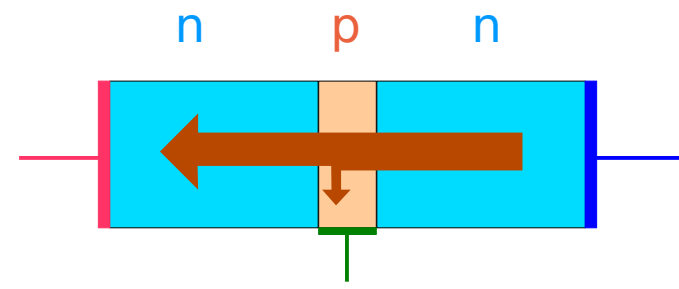

# Common Emitter (1)

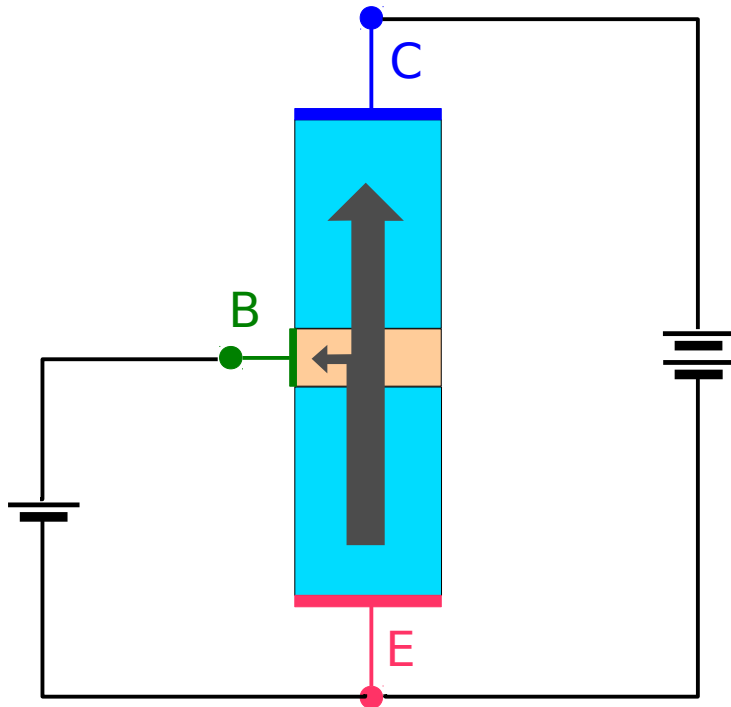


*Electron Flow*


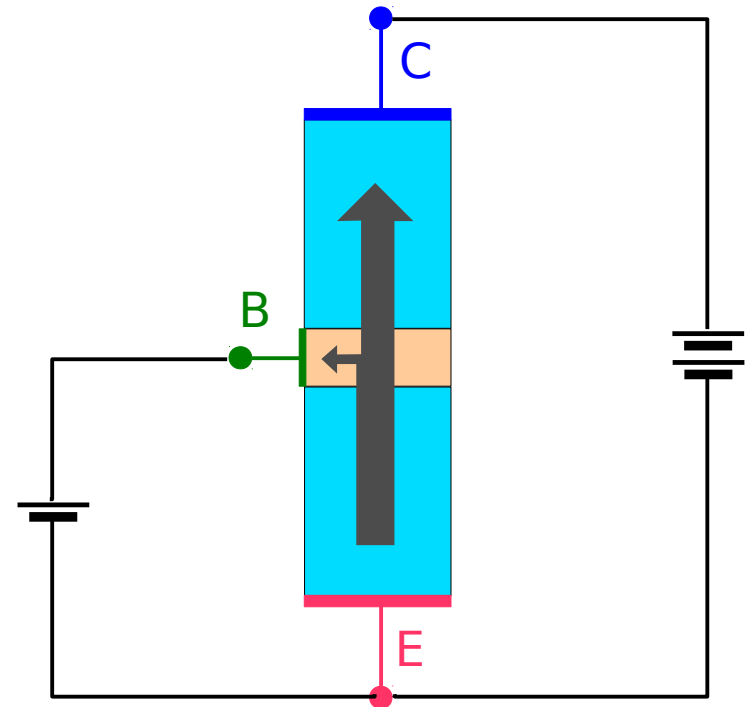


*Current Flow*


# Common Emitter (2)

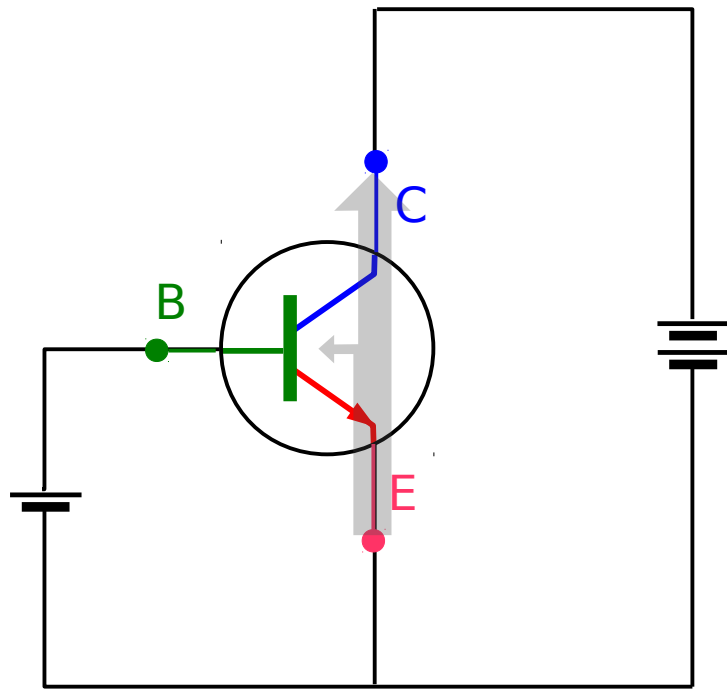


*Electron Flow*

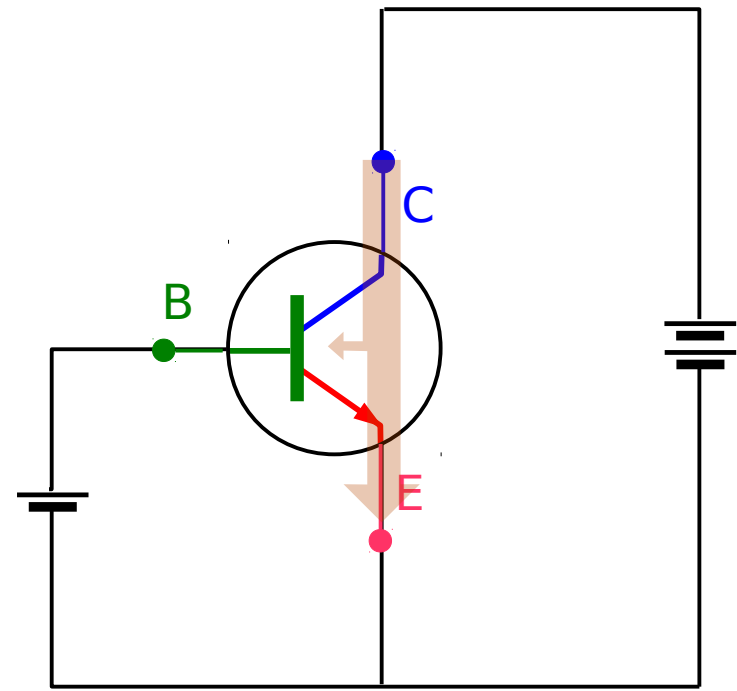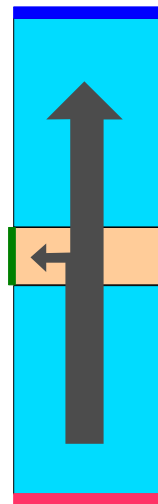


*Current Flow*

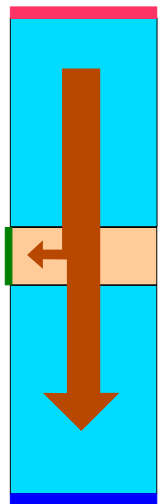


# Common Emitter (2)

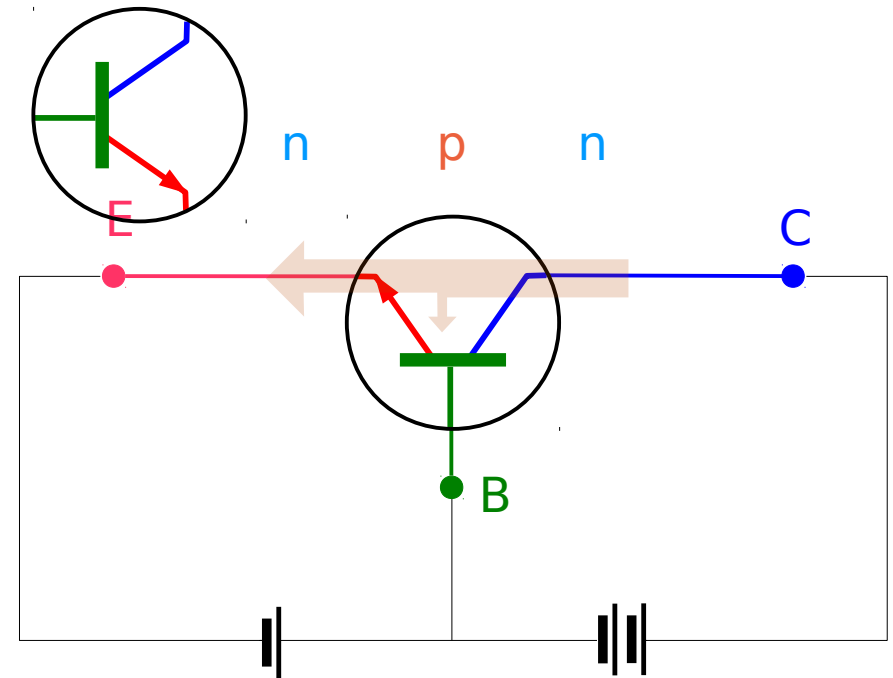

*Electron Flow*

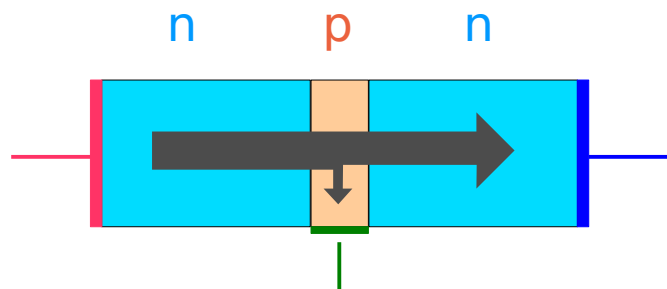


*Current Flow*

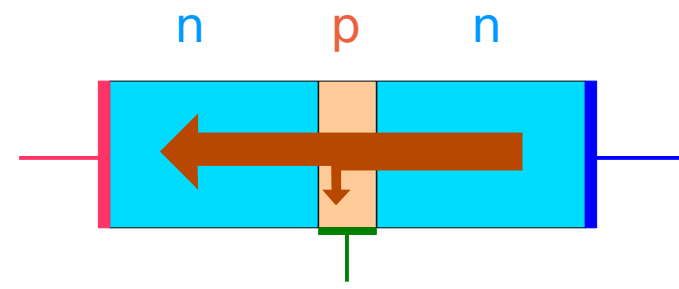


# Maintain Magnetic Field

*Before*

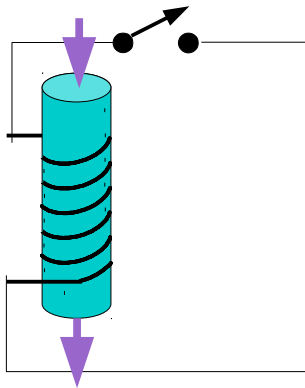


*Initial*

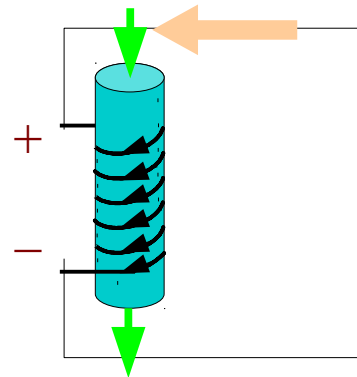

*Induced EMF*


*Final*

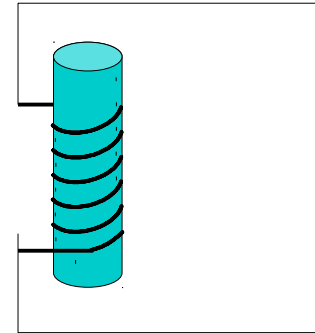


*No Energy in magnetic field*




# Storing Magnetic Energy

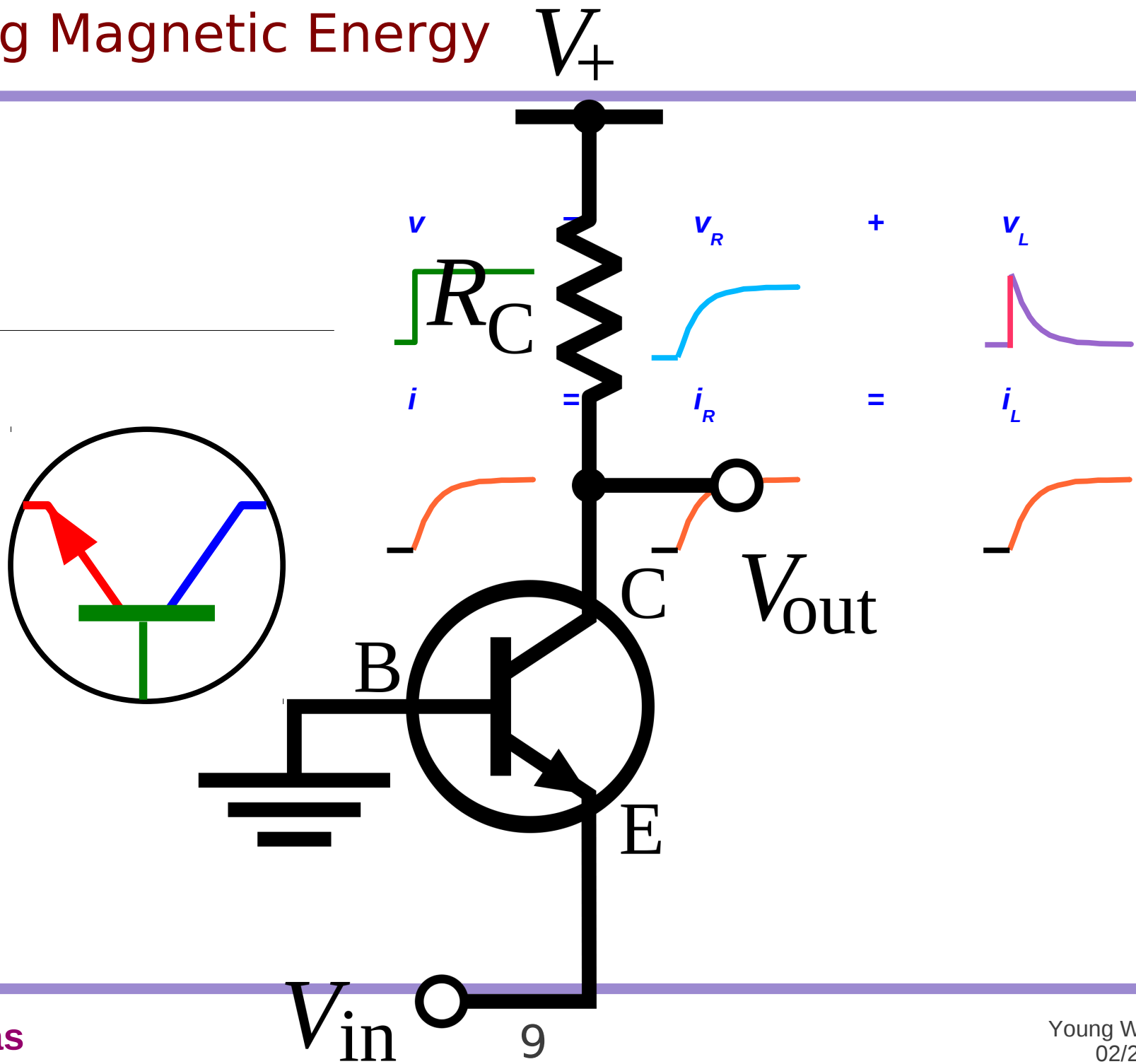


# Dissipate Magnetic Energy

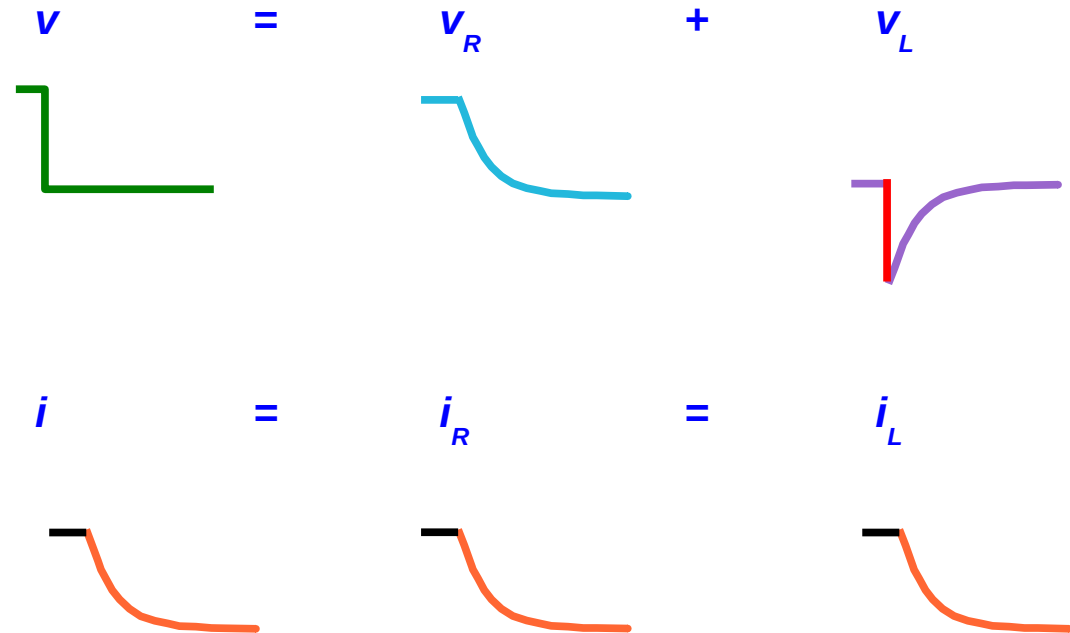

# Pulse


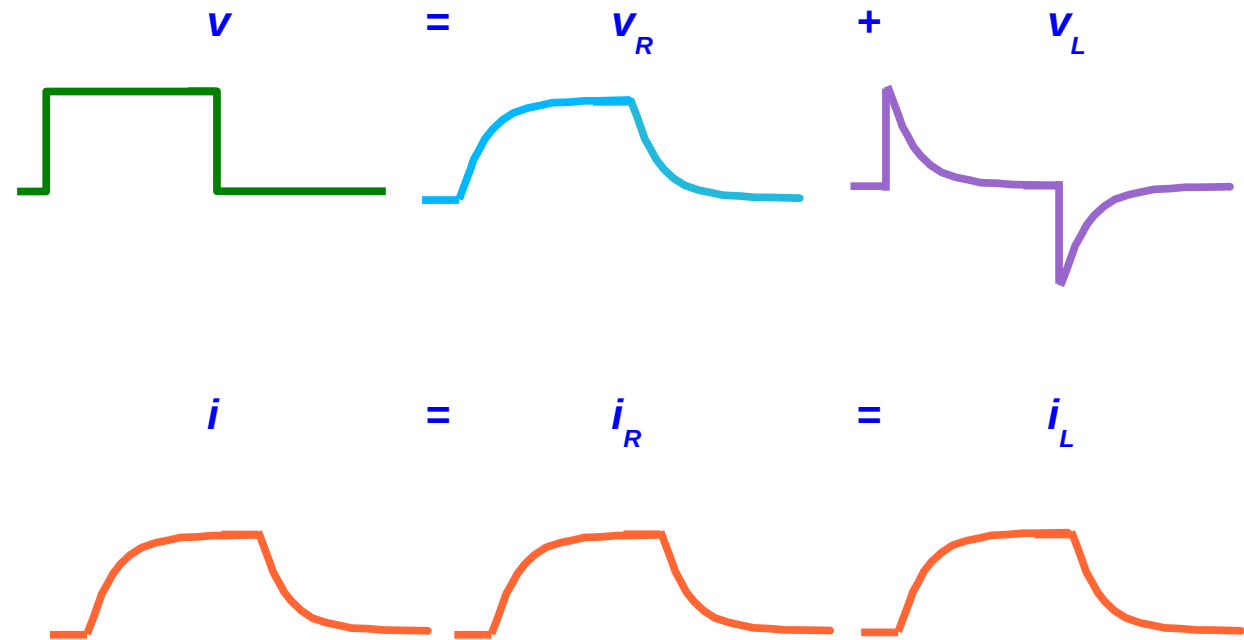


# Pulse

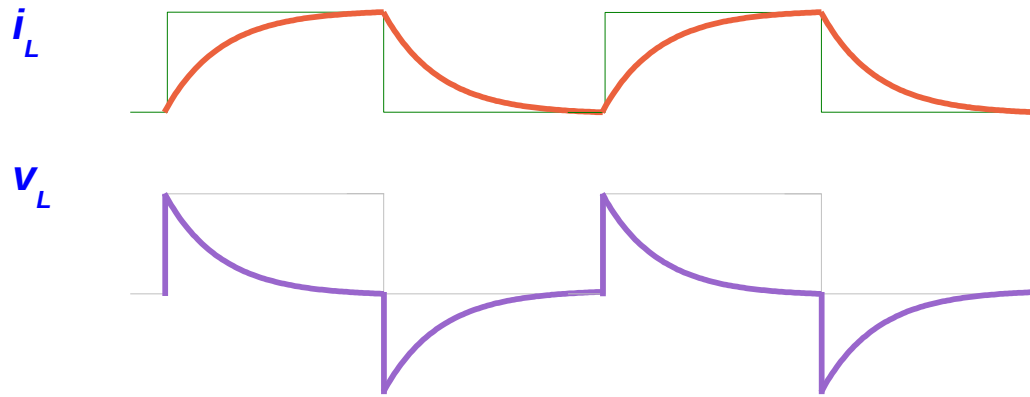

$$v_L = L \frac{di_L}{dt}$$

$\omega$  ↑    $v_L$  ↓    $X_L$  ↑

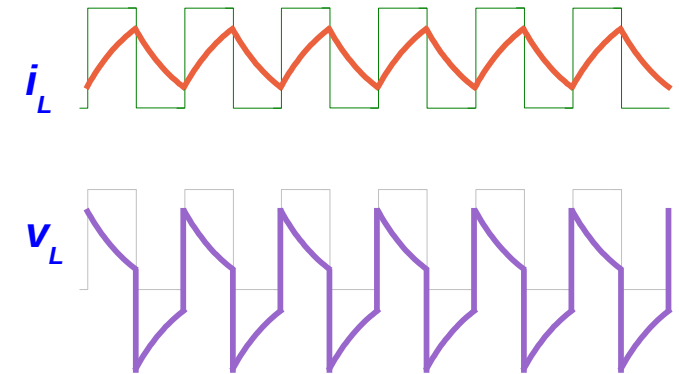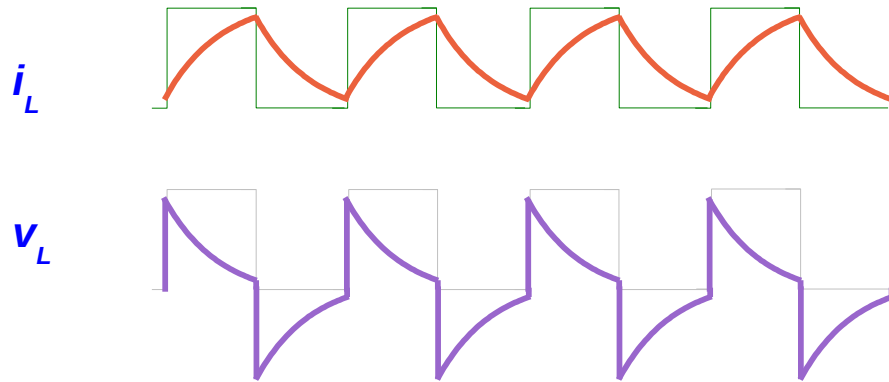

# Phasor

## **Sinusoid (Sine Waves)**

$$A \cos(\omega t + \theta)$$

$$\left\{ \begin{array}{ll} \text{Amplitude} & A \\ \text{Angular Frequency} & \omega \\ \text{Angular Frequency} & \theta \end{array} \right.$$

### 1. Representation using Euler's Formula

$$A \cos(\omega t + \theta) = \frac{A}{2} \cdot e^{+i(\omega t + \theta)} + \frac{A}{2} \cdot e^{-i(\omega t + \theta)}$$

### 2. Representation using Real Part

$$A \cos(\omega t + \theta) = \operatorname{Re}\{A e^{i(\omega t + \theta)}\} = \operatorname{Re}\{A e^{i\theta} \cdot e^{i\omega t}\}$$

$$\rightarrow A e^{i\theta} \cdot e^{i\omega t}$$

$$\rightarrow A e^{i\theta}$$

$$\rightarrow A \angle \theta$$

# Phase Lags and Leads

$$\frac{d}{d x} f(x) = \cos(x) \quad \text{leads} \quad f(x) = \sin(x)$$

$$\frac{d}{d x} f(x) = -\sin(x) \quad \text{leads} \quad f(x) = \cos(x)$$

$$\int f(x) dx = -\cos(x) + C \quad \text{lags} \quad f(x) = \sin(x)$$

$$\int f(x) dx = \sin(x) + C \quad \text{lags} \quad f(x) = \cos(x)$$

$$\frac{d}{d x} f(x) \quad \text{leads} \quad f(x) \quad \text{by} \quad \frac{\pi}{2}$$

$$\int f(x) dx \quad \text{lags} \quad f(x) \quad \text{by} \quad \frac{\pi}{2}$$

## References

[1] <http://en.wikipedia.org/>

[2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003