
Lesson 3: Electronics & Circuits

Preparation for
Amateur Radio
Technician Class
Exam


Topics

- Review
- Ohm's Law
- Energy & Power
- Circuits
- Inductors & Inductance
- Capacitors & Capacitance
- Analog vs Digital
- Exam Questions for this section

Reading



➤ Chapter 7 – 7.11-7.25

A Quick Review!

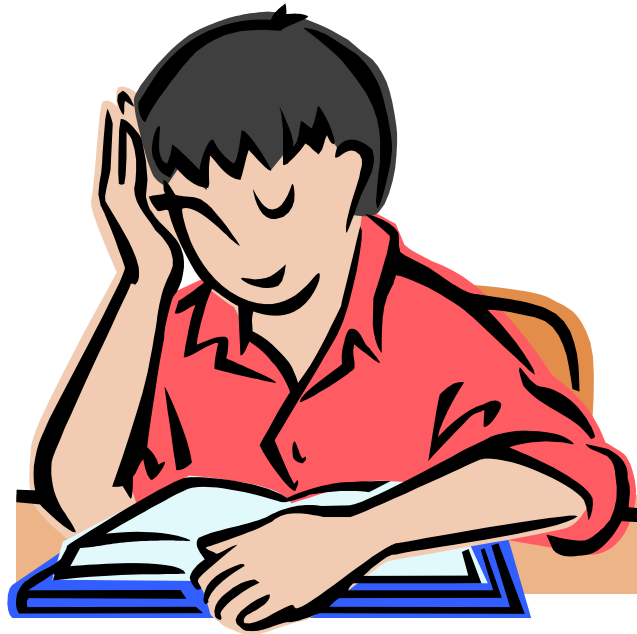


Electricity

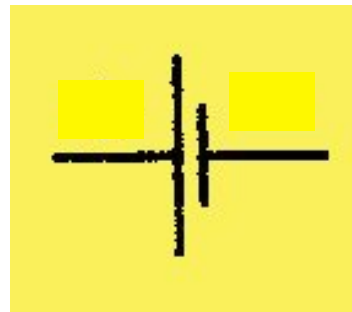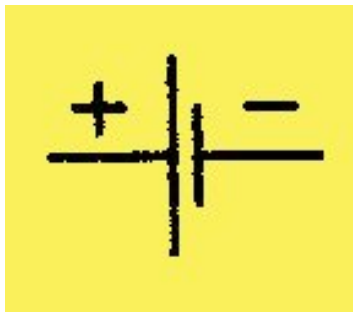- We can diagram electrical circuits using symbols
- A single cell battery, such as a small hearing aid or watch battery, has this symbol on an electrical diagram:





Resistance

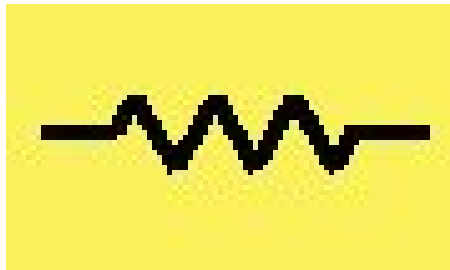- Since a resistor is a part of an electrical circuit, we can diagram it. Here is a fixed and 2 versions of variable resistors:



Fixed

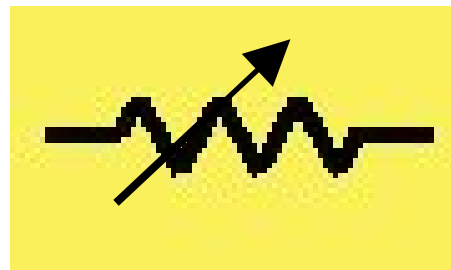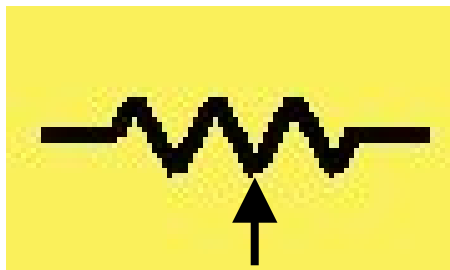


Variable resistors
or pots

Series & Parallel Circuits

- Series – the parts are connected in a line and the current flows through each part in turn
- In a series circuit, add all the resistor values together, as if it were one large resistor, rather than several smaller ones
- Total resistance is the sum of the values of the resistors:


$$R_{\text{total}} = R1 + R2 + R3$$

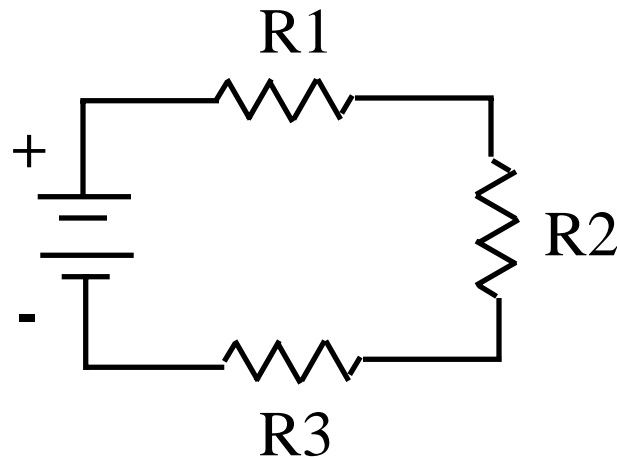

Series & Parallel Circuits

- Parallel – the parts are connected so that current flows through all the parts at the same time
- This reduces the effect of each individual resistor, so the combination appears to have a smaller value
- Total resistance is one over the sum of the inverse of the values of the resistors:
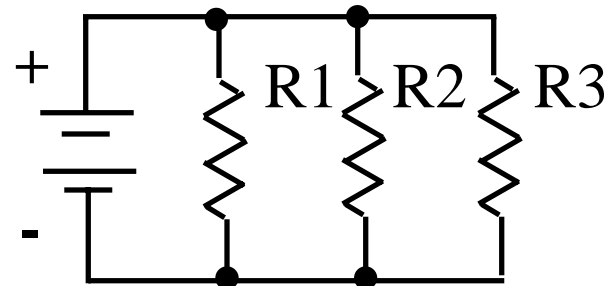
$$R_{\text{total}} = \frac{1}{\frac{1}{R1} + \frac{1}{R2} + \frac{1}{R3}}$$



Electricity

- We learned that electricity is measured by current, which is the flow of electrons
 - Current is measured in amps
 - Amps are measured with an ammeter or amp meter
- Current or Amps in electricity is analogous to current in a river

Electricity



- It takes force to make the electrons move
- This is called the Electromotive force
 - It is measured in volts (V)
 - Volts are measured with a voltmeter
- Force or Volts in electricity is analogous to a waterfall
 - The height of the waterfall determines the force when the water hits the bottom
 - The volts in electricity determine the force pushing the current

Resistance

- Resistance is what prevents electricity from moving through an electrical circuit
 - Think of water flowing through a pipe
 - The smaller you make the pipe, the more resistance there is to water going through, so the less water goes through
 - Or think of a small pebble stuck in the pipe, preventing some amount of the water from getting through


Ohm's Law

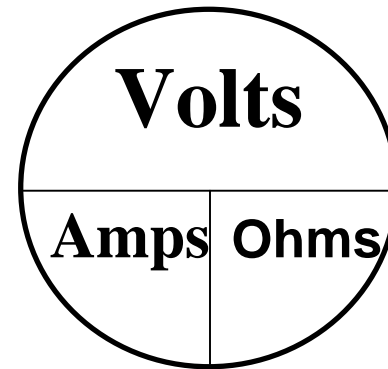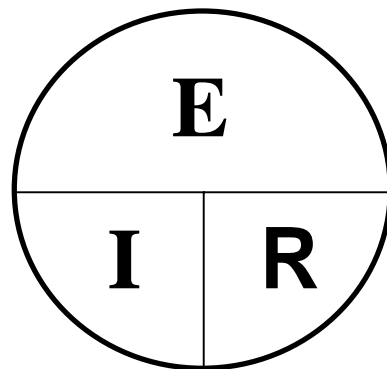- Ohm's law relates the electrical current to the voltage and resistance
 - E = Electromotive force that is measured in Volts
 - I = Intensité (current) measured in amps
 - R = Resistance measured in Ohms (written Ω)




Ohm's Law

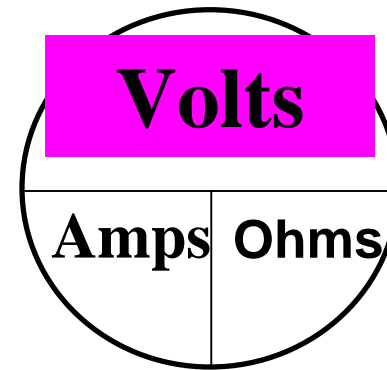- Given current and resistance, you can find force
 - Volts = amps * Ohms
 - If a current of 2 amperes flows through a 50-ohm resistor, what is the voltage across the resistor?
 - $100 \text{ Volts} = 2 \text{ amps} * 50 \Omega$




Ohm's Law

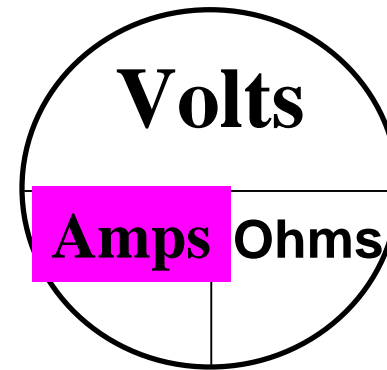- Given resistance and force, you can find current
 - $\text{amps} = \text{Volts} / \text{Ohms}$
 - If a 100-ohm resistor is connected to 200 volts, what is the current through the resistor?
 - $2 \text{ amps} = 200 \text{ volts} / 100 \Omega$



Ohm's Law

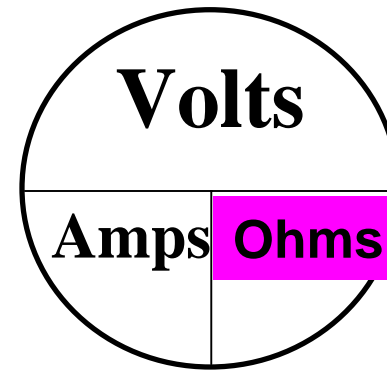- Given current and force, you can find resistance
 - Ohms = Volts / amps
 - If a current of 3 amperes flows through a resistor connected to 90 volts, what is the resistance?
 - $30 \Omega = 90 \text{ volts} / 3 \text{ amps}$



Energy & Power

- Energy is the ability to do work
- Power is the rate of energy consumption
- We measure electrical power in Watts
- Decibels (dB) are used to compare power levels
 - Note that dB is not an absolute value, but a comparison of two values
 - $\text{dB} = \log (\text{new watts} / \text{original watts}) * 10$
- This can indicate an increase or decrease in power

Energy & Power

- Increase your power output from 5 watts to 10 watts – what is the dB change?
 - $\text{dB} = \log (\text{new watts} / \text{original watts}) * 10$
 - $\text{dB} = \log (10 / 5) * 10 = (0.3) * 10 = 3 \text{ dB}$


Circuits

➤ Switch


- Controls a circuit
- A switch is open or closed (off or on)

➤ There are several kinds of switches, each with their own symbol

Single-pole, double-throw

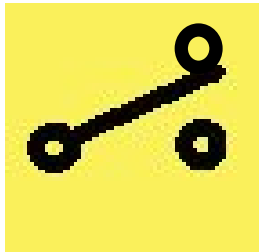

Double-pole, single-throw

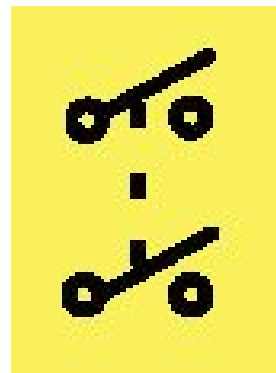


Circuits

➤ Antenna

- Moves RF from the air to the receiver and from the transmitter to the air

➤ This is the symbol for an antenna:

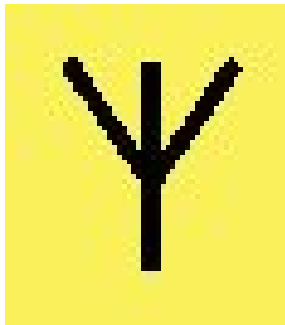


Circuits

➤ Diodes

- Allow current to flow in only one direction through the circuit
- Can be used to change an alternating current signal into a varying direct current signal – called rectifying the signal, so sometimes a diode is called a rectifier

➤ This is the symbol for a diode:

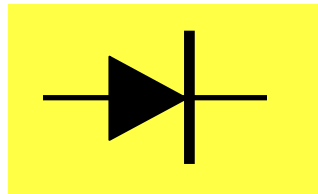

Circuits


➤ Transistor

- Amplifies a small signal
- Uses low voltage
 - By contrast a vacuum tube amplifies a small signal, but uses high voltage to do so
- Come in two main types : PNP, NPN

➤ The symbols for transistors are:

PNP

Points in proudly

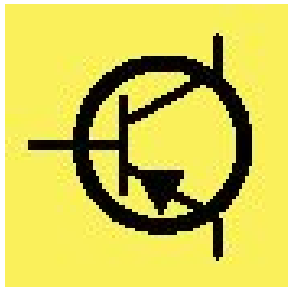

NPN


Not pointing in



Circuits

➤ Integrated Circuits

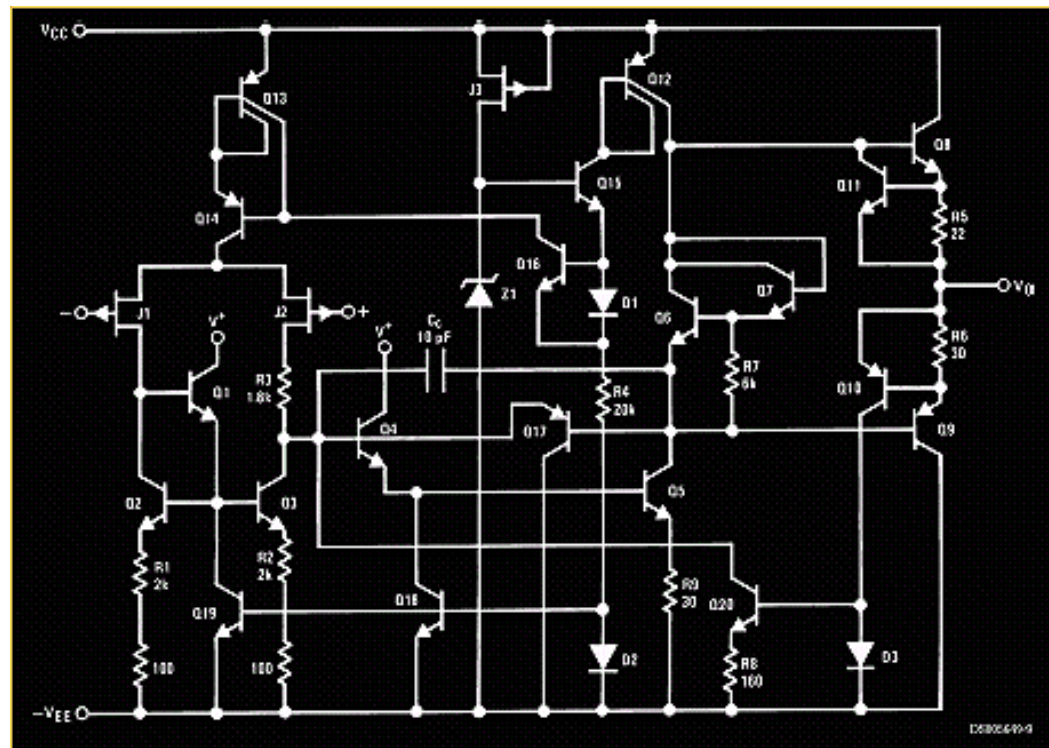- Combine several circuit functions in one package




Inductors & Inductance

➤ Inductor

- Stores energy in an electro-magnetic field
 - The flow of electricity through a wire creates a magnetic field around the wire
 - An inductor is a coil of wire that has a magnetic field when electricity is applied to it
 - Some also have an iron or ferrite core
- An inductor resists changes in current, evening out the flow of electricity through the circuit
- Inductance is measured in Henry's

Inductors & Inductance

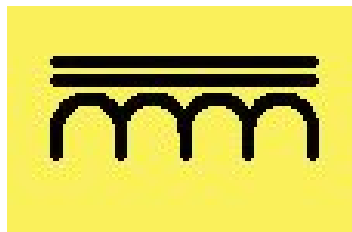
- Inductors can have fixed or variable values, an air core, iron core, or other kind of core
- The symbol for a fixed value iron core inductor is this:



Capacitors & Capacitance

➤ Capacitor

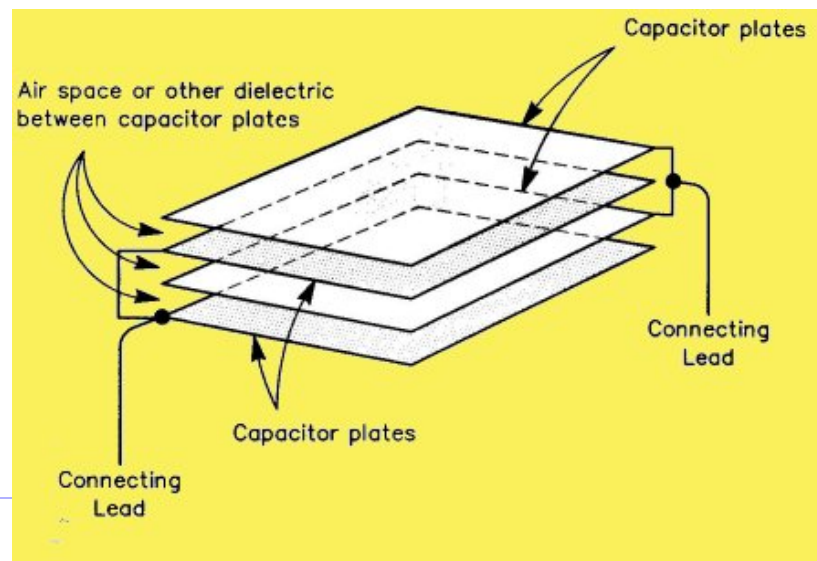- Blocks the flow of direct current, but allows alternating current to pass
- Stores energy in an electrostatic field and opposes a change in voltage
- Capacitance is measured in farads




Capacitors & Capacitance

➤ Capacitor

- Some capacitors have fixed values, others are variable
 - Variable capacitors are: two sets of rotating conducting plates separated by an insulator, which can be varied in surface area exposed to each other

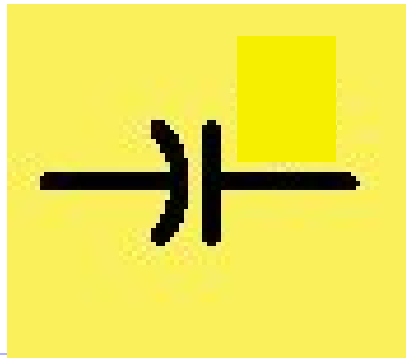➤ The symbol for a fixed value capacitor is:



Capacitors & Capacitance

- Capacitors can be connected in series or parallel, in the same way that resistors can be connected in series or parallel
 - When **resistors** are connected in **series**, we sum their values
 - When **capacitors** are connected in **parallel**, we sum their values
 - So 2 equal valued capacitors connected in parallel have twice the capacitance of one

Analog vs Digital

- Analog signals have voltage or current values that vary continuously over some range
- Examples of analog communication signals include:
 - FM voice
 - SSB voice
 - SSTV
 - ATV

Analog vs Digital

- Digital signals have voltage or current in specified steps over some range
 - Typically only two steps, on and off
- Examples of digital signals include:
 - RTTY
 - Packet
 - Morse code

Exam Questions

- The following slides contain questions from the exam pool that are covered in this section of the notes

T7A12

- T7A12 What formula shows how voltage, current and resistance relate to each other in an electric circuit?
- A. Ohm's Law
 - B. Kirchhoff's Law
 - C. Ampere's Law
 - D. Tesla's Law

T7A13

- T7A13 If a current of 2 amperes flows through a 50-ohm resistor, what is the voltage across the resistor?
- A. 25 volts
 - B. 52 volts
 - C. 100 volts
 - D. 200 volts

T7A14

- T7A14 If a 100-ohm resistor is connected to 200 volts, what is the current through the resistor?
- A. 1 ampere
 - B. 2 amperes
 - C. 300 amperes
 - D. 20,000 amperes

T7A15

- T7A15 If a current of 3 amperes flows through a resistor connected to 90 volts, what is the resistance?
- A. 3 ohms
 - B. 30 ohms
 - C. 93 ohms
 - D. 270 ohms

T7A04

- T7A04 What is the basic unit of electrical power?
- A. The ohm
 - B. The watt
 - C. The volt
 - D. The ampere

T7A16

- T7A16 If you increase your transmitter output power from 5 watts to 10 watts, what decibel (dB) increase does that represent?
- A. 2 dB
 - B. 3 dB
 - C. 5 dB
 - D. 10 dB

T7A11

- T7A11 Which of the following circuits changes an alternating current signal into a varying direct current signal?
- A. Transformer
 - B. Rectifier
 - C. Amplifier
 - D. Director

T7B10

- T7B10 Which component can amplify a small signal using low voltages?
- A. A PNP transistor
 - B. A variable resistor
 - C. An electrolytic capacitor
 - D. A multiple-cell battery

T7B11

- T7B11 Which component can amplify a small signal but normally uses high voltages?
- A. A transistor
 - B. An electrolytic capacitor
 - C. A vacuum tube
 - D. A multiple-cell battery

T7C09

- T7C09 What component controls current to flow in one direction only?
- A. A fixed resistor
 - B. A signal generator
 - C. A diode
 - D. A fuse

T7C10

- T7C10 What is one advantage of using ICs (integrated circuits) instead of vacuum tubes in a circuit?
- A. ICs usually combine several functions into one package
 - B. ICs can handle high-power input signals
 - C. ICs can handle much higher voltages
 - D. ICs can handle much higher temperatures

T7C14

- T7C14 In Figure T7-1, which symbol represents an NPN transistor?
- A. Symbol 2
 - B. Symbol 4
 - C. Symbol 10
 - D. Symbol 12

T7C16

- T7C16 In Figure T7-1, which symbol represents an antenna?
- A. Symbol 5
 - B. Symbol 7
 - C. Symbol 8
 - D. Symbol 14

T7C18

- T7C18 In Figure T7-2, which symbol represents a single-pole, double-throw switch?
- A. Symbol 1
 - B. Symbol 2
 - C. Symbol 3
 - D. Symbol 4

T7C19

- T7C19 In Figure T7-2, which symbol represents a double-pole, single-throw switch?
- A. Symbol 1
 - B. Symbol 2
 - C. Symbol 3
 - D. Symbol 4

T7A09

- T7A09 What is the basic unit of inductance?
- A. The coulomb
 - B. The farad
 - C. The henry
 - D. The ohm

T7C08

- T7C08 What does an inductor do?
- A. It stores energy electrostatically and opposes a change in voltage
 - B. It stores energy electrochemically and opposes a change in current
 - C. It stores energy electromagnetically and opposes a change in current
 - D. It stores energy electromechanically and opposes a change in voltage

T7C17

- T7C17 In Figure T7-1, which symbol represents a fixed-value iron-core inductor?
- A. Symbol 6
 - B. Symbol 9
 - C. Symbol 11
 - D. Symbol 12

T7A10

- T7A10 What is the basic unit of capacitance?
- A. The farad
 - B. The ohm
 - C. The volt
 - D. The henry

T7C04

- T7C04 What is one reason capacitors are used in electronic circuits?
- A. To block the flow of direct current while allowing alternating current to pass
 - B. To block the flow of alternating current while allowing direct current to pass
 - C. To change the time constant of the applied voltage
 - D. To change alternating current to direct current

T7C05

- T7C05 If two equal-value capacitors are connected in parallel, what is their total capacitance?
- A. Twice the value of one capacitor
 - B. Half the value of one capacitor
 - C. The same as the value of either capacitor
 - D. The value of one capacitor times the value of the other

T7C06

- T7C06 What does a capacitor do?
- A. It stores energy electrochemically and opposes a change in current
 - B. It stores energy electrostatically and opposes a change in voltage
 - C. It stores energy electromagnetically and opposes a change in current
 - D. It stores energy electromechanically and opposes a change in voltage

T7C07

- T7C07 Which of the following best describes a variable capacitor?
- A. A set of fixed capacitors whose connections can be varied
 - B. Two sets of insulating plates separated by a conductor, which can be varied in distance from each other
 - C. A set of capacitors connected in a series-parallel circuit
 - D. Two sets of rotating conducting plates separated by an insulator, which can be varied in surface area exposed to each other

T7C15

- T7C15 Which symbol of Figure T7-1 represents a fixed-value capacitor?
- A. Symbol 1
 - B. Symbol 3
 - C. Symbol 5
 - D. Symbol 13

T7B01

- T7B01 What type of electric circuit uses signals that can vary continuously over a certain range of voltage or current values?
- A. An analog circuit
 - B. A digital circuit
 - C. A continuous circuit
 - D. A pulsed modulator circuit

T7B02

- T7B02 What type of electric circuit uses signals that have voltage or current values only in specific steps over a certain range?
- A. An analog circuit
 - B. A digital circuit
 - C. A step modulator circuit
 - D. None of these choices is correct

T7B03

- T7B03 Which of the following is an example of an analog communications method?
- A. Morse code (CW)
 - B. Packet Radio
 - C. Frequency-modulated (FM) voice
 - D. PSK31

T7B04

- T7B04 Which of the following is an example of a digital communications method?
- A. Single-sideband (SSB) voice
 - B. Amateur Television (ATV)
 - C. FM voice
 - D. Radioteletype (RTTY)