

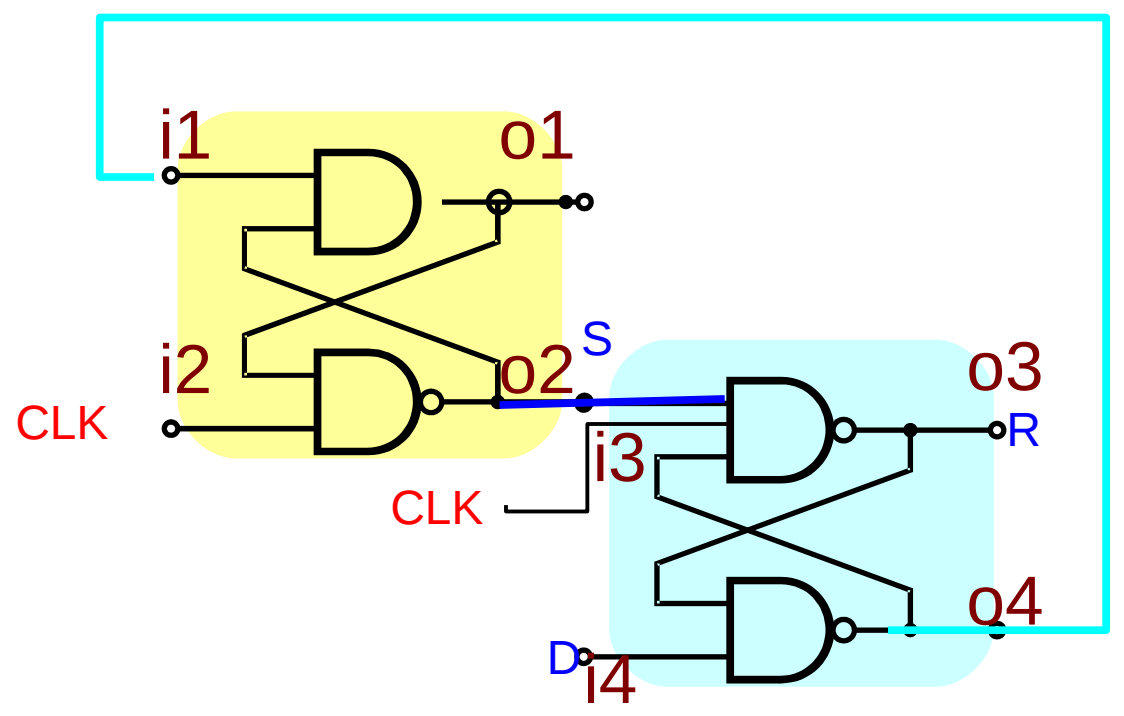



Output Stage Latch

Input Stage Latch

 

 


Output Stage Latch

 


	CLK=0	CLK=0 → 1	CLK= 1
	S=1 R=1	When D=0 S=1 R=0 When D=1 S=0 R=1	When D=0 → 1 S=1 R=0 When D=1 → 0 S=0 R=1
	Maintain output latch	D=0/1 at the rising edge reset / set the output latch	Maintain reset / set at the rising edge regardless of input changes

Input Stage Latch – CLK = 0

 

SR=11


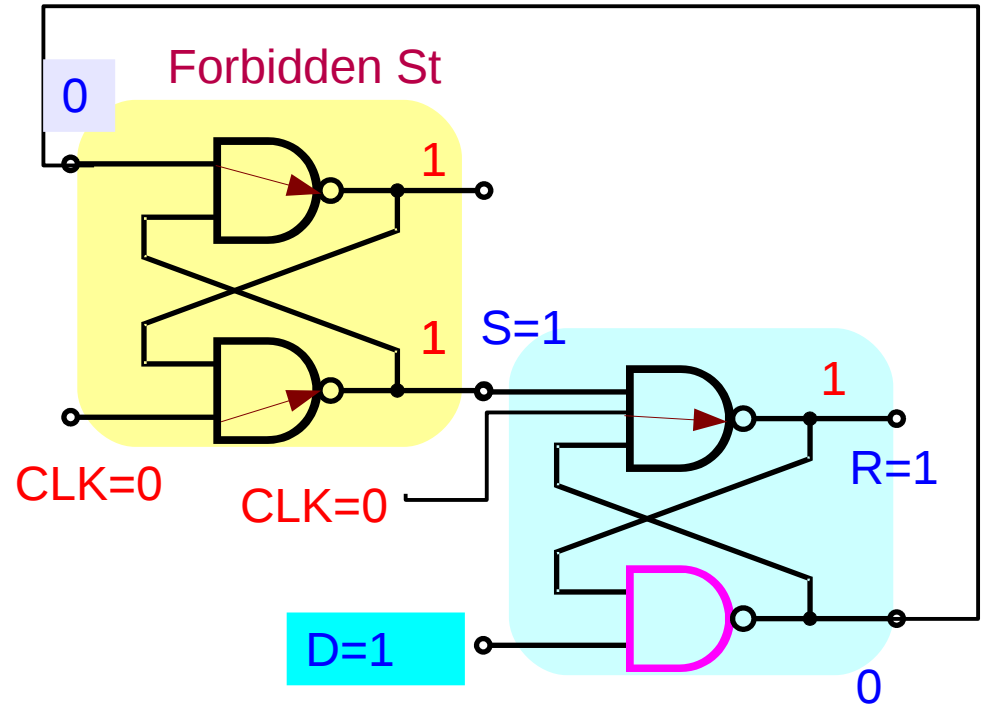


If the clock is low, both the output signals of the input stage are high regardless of the data input; the output latch is unaffected and it stores the previous state.

Input Stage Latch – Rising Edge

$D=0 \rightarrow SR=10$

$D=1 \rightarrow SR=01$

  

When the clock signal changes from low to high, (rising edge) only one of the output voltages (S or R) goes low (depending on the data signal D) and sets/resets the output latch:

($D=0 \rightarrow SR = 10 \rightarrow$ reset the output latch $\rightarrow Q= 0$)

($D=1 \rightarrow SR = 01 \rightarrow$ set the output latch $\rightarrow Q = 1$)



if $D = 0$, the lower output becomes low ; (Reset operation $SR=10$)

if $D = 1$, the upper output becomes low. (Set operation $SR=01$)

Input Stage Latch – CLK=1

$D=(0 \rightarrow 1) \rightarrow SR=10$

$D=(1 \rightarrow 0) \rightarrow SR=01$

 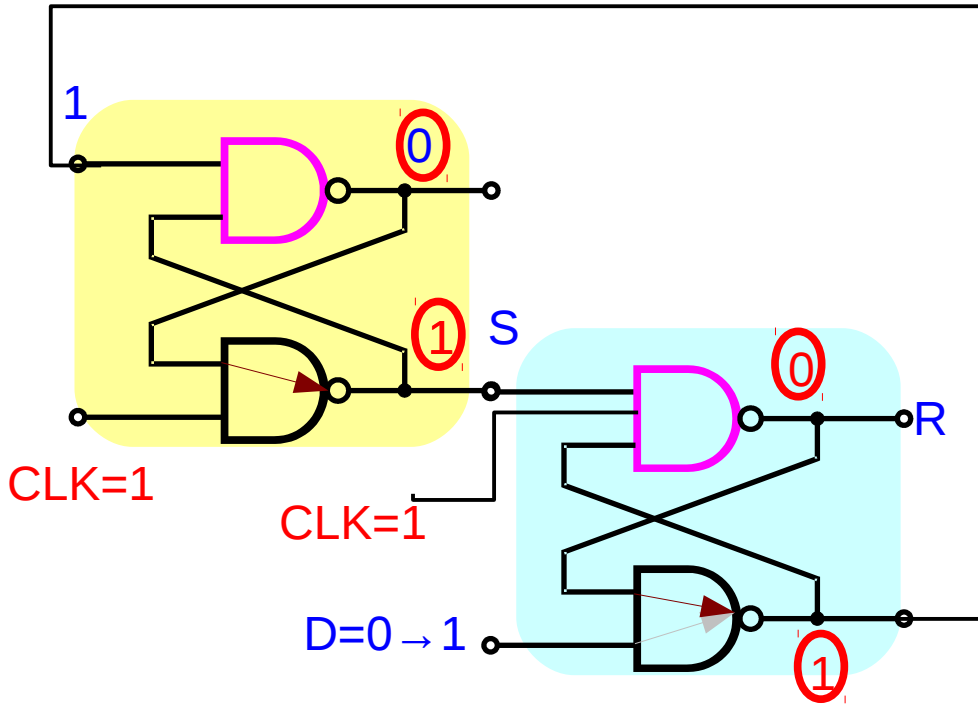

If the clock signal continues staying **high**, the outputs keep their states regardless of the data input ($D=0$: $SR=10$, $D=1$: $SR=01$ at the rising edge) and force the output latch to stay in the corresponding state as the input logical zero remains active ($SR=10$: Reset, $SR=01$: Set) while the clock is **high**.

If the clock signal continues staying high, the outputs keep their states regardless of the data input and force the output latch to stay in the corresponding state as the input logical zero remains active while the clock is high.

Hence the role of the output latch is to store the data only while the clock is low.

The input stage (the two latches on the left)
processes the clock and data signals
to ensure correct input signals
for the output stage (the single latch on the right).

The circuit is closely related to the gated D latch as both the circuits

convert the **two D input states** (0 and 1) **D**
to **two input combinations** (10 and 01) **SR**

for the output SR latch

by inverting the data input signal


(both the circuits split the single D signal
in two complementary S and R signals).

The difference is that

in the gated D latch, simple NAND logical gates are used
while in the positive-edge-triggered D flip-flop SR NAND latches
are used for this purpose.

The role of these latches is to "lock" the active output producing
low voltage (a logical zero); thus the positive-edge-triggered D flip-
flop can be thought of as a gated D latch with latched input gates.

NAND RS Latch

 

$S' = 0$
 $R' = 1$

$S' = 1$
 $R' = 0$

$S' = 0$
 $R' = 1$


$S' = 1$
 $R' = 0$

$S' = 1$
 $R' = 1$

$S' = 1$
 $R' = 1$

$S' = 1$
 $R' = 1$

$S' = 1$
 $R' = 1$

 

CLK=0

L1 in Reset

L1 in forbidden

if P=0

if P=1

L2 in Set if D=1


S=1, R=1,
P=0

X

L2 in forbidden if D=0


X

S=1, R=1,
P=1

 



CLK=1		L1 in Set if $P=0$	L1 in Hold if $P=1$
L2 in Set	if $S=0, D=1$	$S=0, R=1, P=0$	X
L2 in Reset	if $S=1, D=0$	X	$S=1, R=0, P=1$
L2 in Hold	if $S=1, D=1$	X	$S=1, R=0, P=1$
L2 in Forbidden	if $S=0, D=0$	X	$S=0, R=1, P=1$

NAND RS Latch

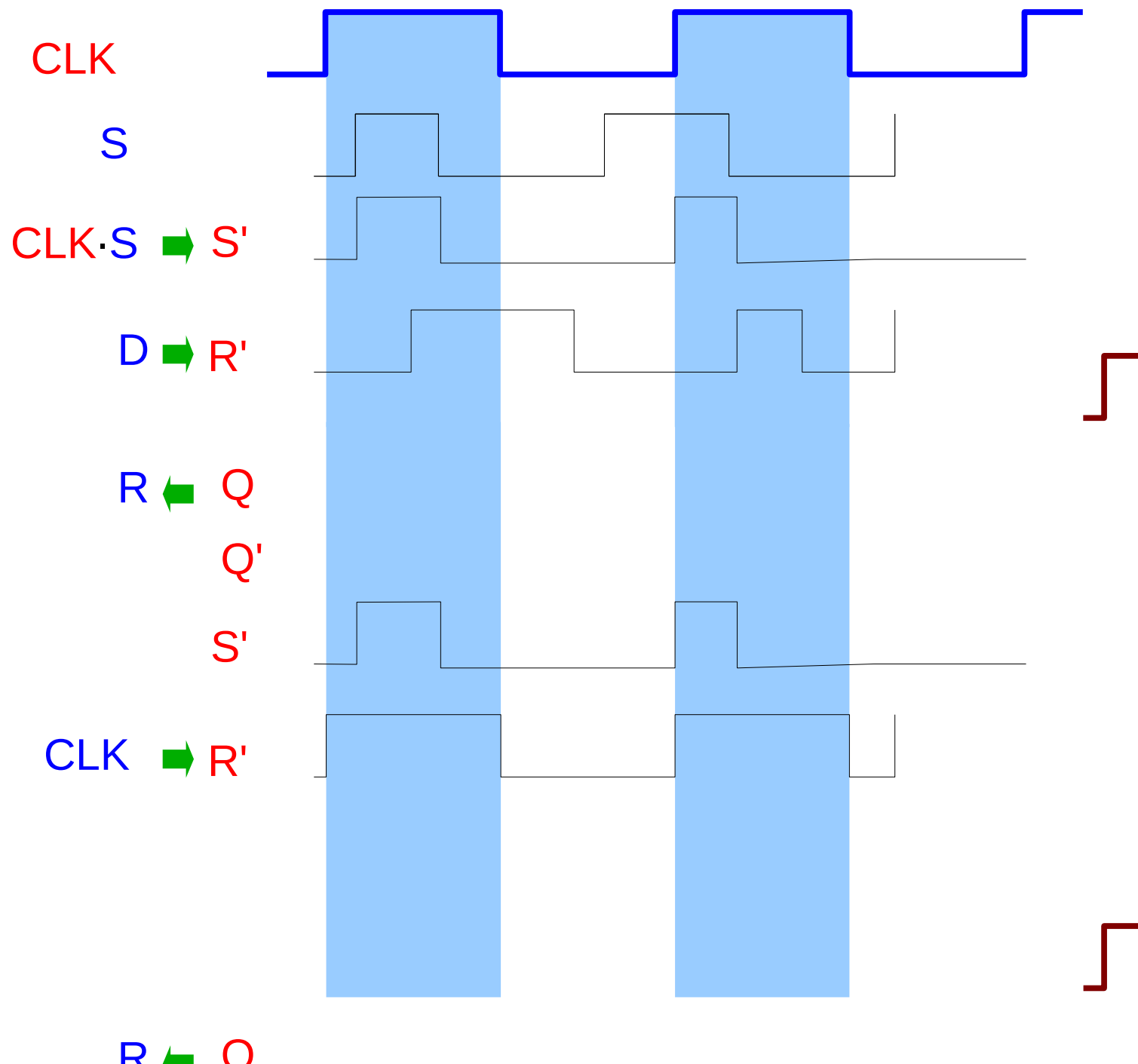


Clocked NOR RS Latch

 


 

SET op for the output latch

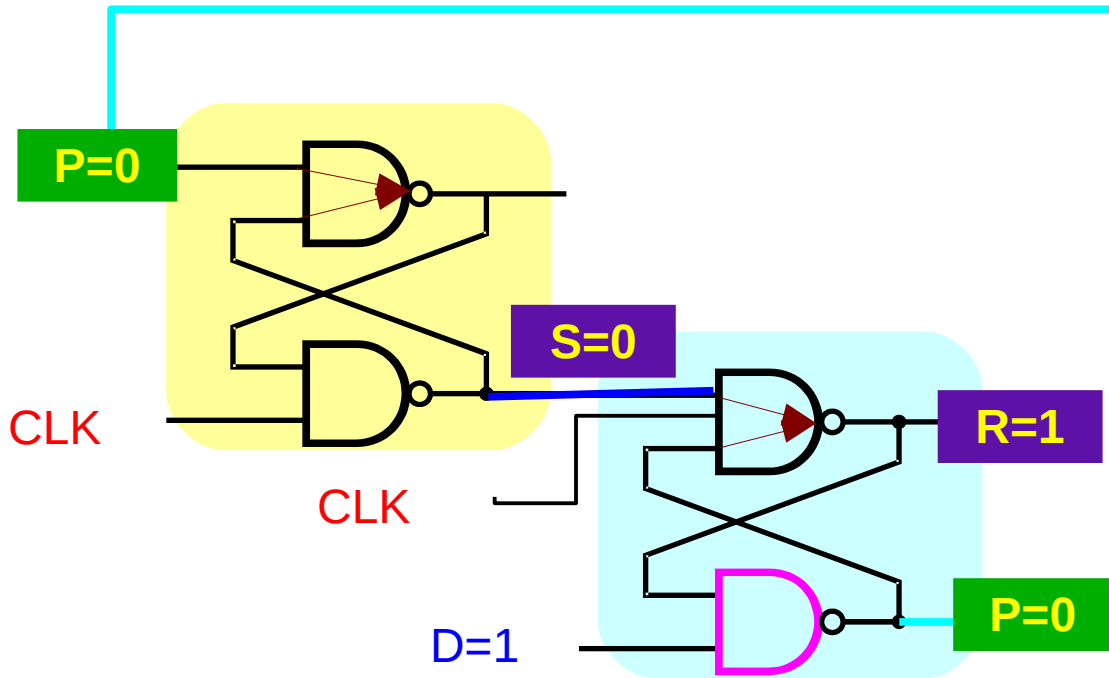


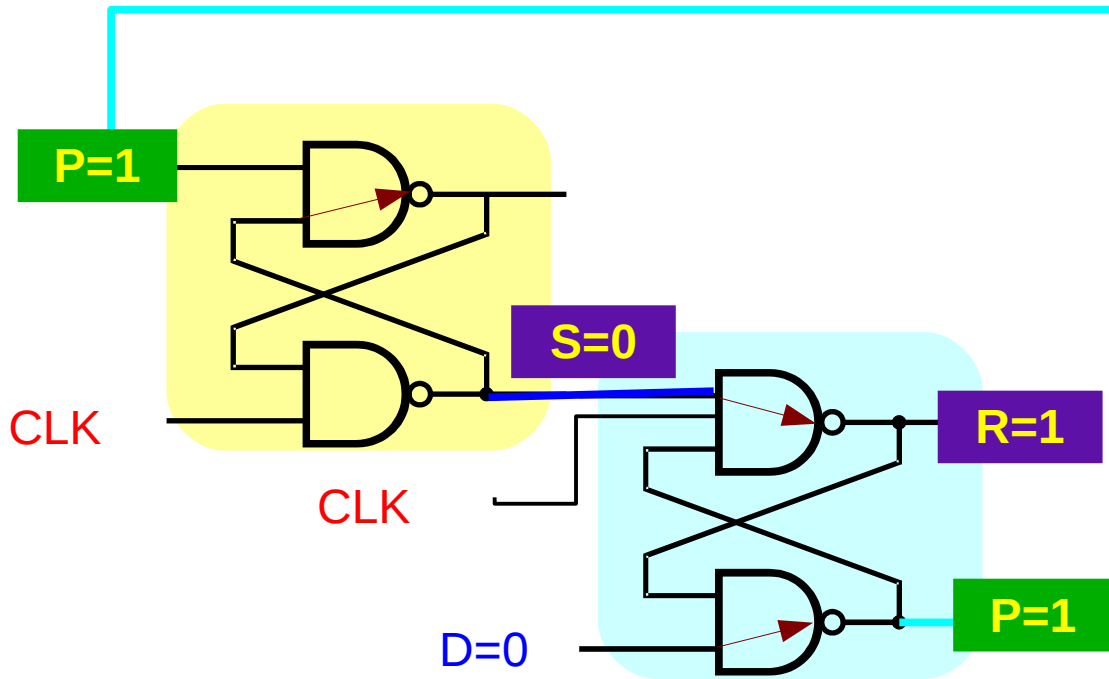$CLK=0 \rightarrow S=1 \rightarrow CLK=1$
 $D=1 \rightarrow P=0$







$CLK=0 \rightarrow S=1 \rightarrow CLK=1$
 $D=0 \rightarrow P=1$

RESET op for the output latch

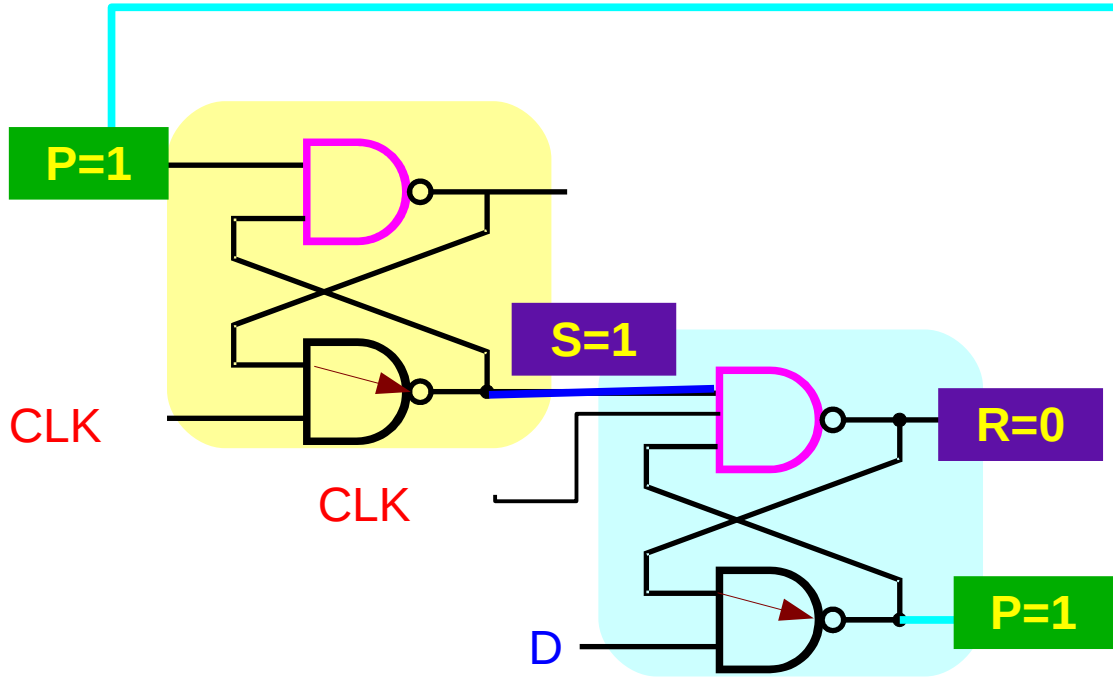

CLK=0 → ~~F=1~~ → CLK=1
D=0 / 1

HOLD op for the output latch

 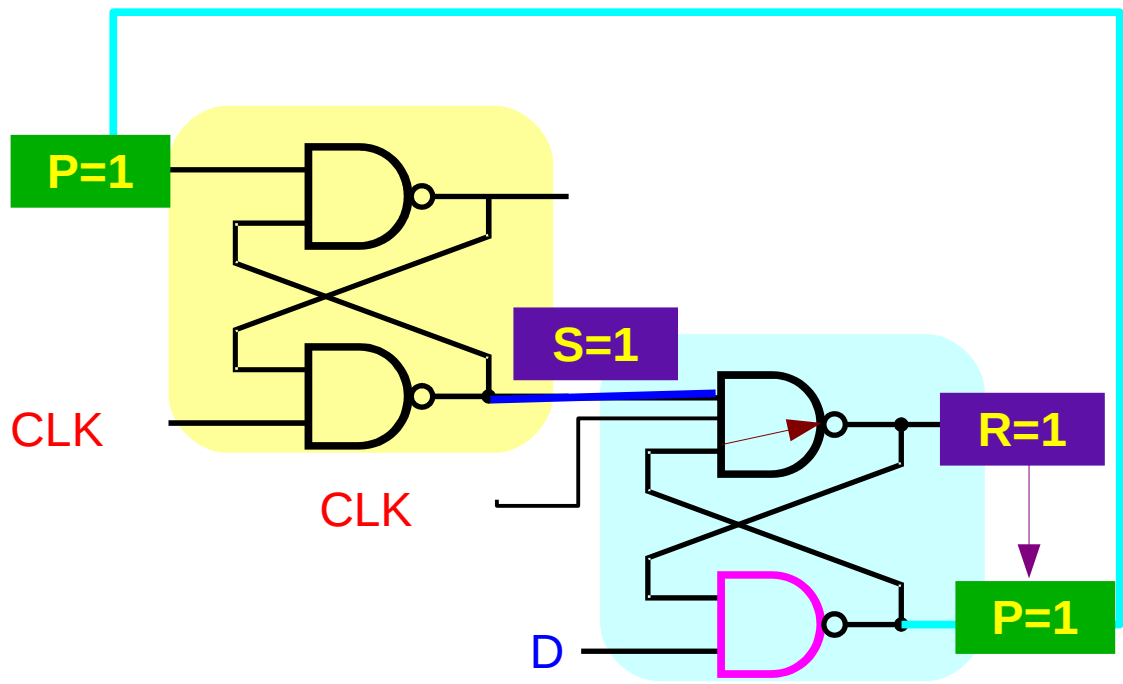 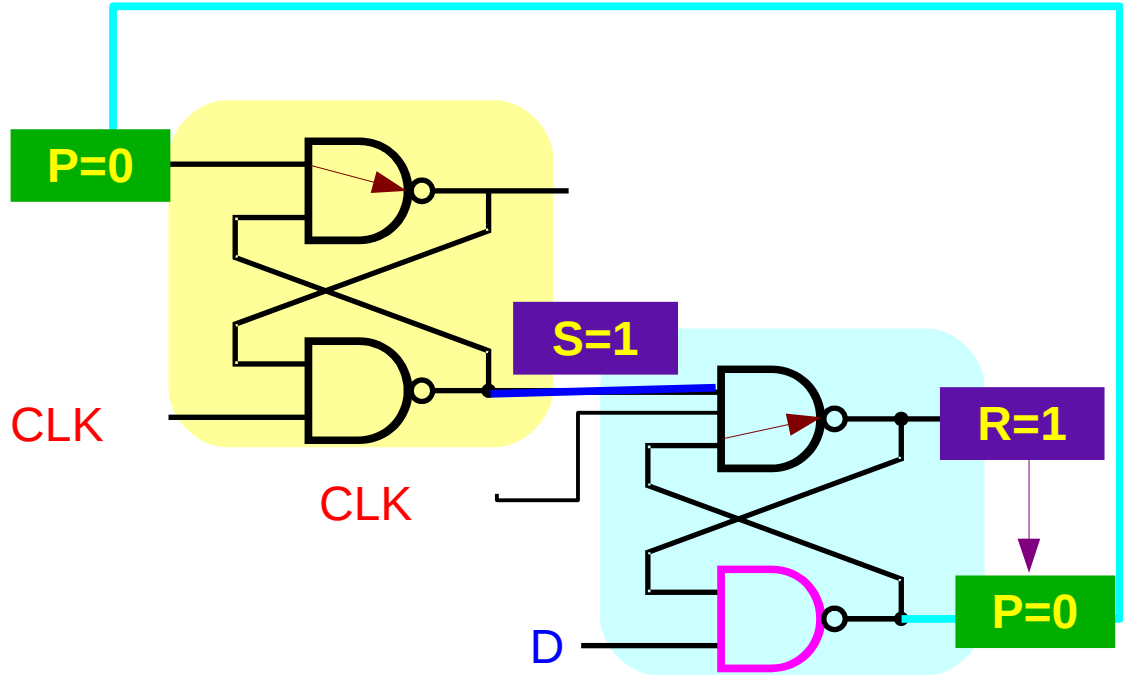

Forbidden op for the output latch

